

IITB-CPU

Guide: Prof. Virendra Singh

EE224 : Digital Design

Team 16

Aaditya Gupta

22B3941

Dattaraj Salunkhe

22B1296

Harsh S Roniyar

22B3942

Pranav Prakash

22B3945

CONTENTS

1	Problem Statement	2
2	Components	2
3	Instruction Set Architecture	3
3.1	Instruction Formats	3
3.2	Instructions Encoding	3
4	State Descriptions	4
4.1	S ₀	4
4.2	S ₁	4
4.3	S ₂	4
4.4	S ₃	4
4.5	S ₄	4
4.6	S ₅	5
4.7	S ₆	5
4.8	S ₇	5
4.9	S ₈	5
4.10	S ₉	5
4.11	S ₁₀	6
4.12	S ₁₁	6
4.13	S ₁₂	6
4.14	S ₁₃	6
5	Instruction State-Flow Diagram	6
5.1	ADD/SUB/MUL/AND/OR/IMP	6
5.2	ADI	6
5.3	LHI	6
5.4	LLI	7
5.5	LW	7
5.6	SW	7
5.7	BEQ	7
5.8	JAL	7
5.9	JLR	7
6	Finite State Machine	8
7	DataPath	9
8	RTL Simulation	9
9	Conclusion	10
10	Member Contributions	10

1 PROBLEM STATEMENT

Design a computing system, IITB-CPU, whose instruction set architecture is provided. Use VHDL as HDL to implement the CPU. IITB-CPU is a 16-bit very simple computer developed for teaching purpose based on the Little Computer Architecture. The IITB-CPU is an 8-register, 16-bit computer system, i.e., it can process 16 bits at a time. It should use point-to-point communication infrastructure.

The IITB-CPU is an 8-register, 16-bit computer system. It has 8 general-purpose registers (R₀ to R₇). Register R₇ always stores the Program Counter (Instruction Pointer). PC points to the next instruction. All addresses are short word addresses. This architecture uses condition code register which has two flags Carry flag (C) and Zero flag (Z). The IITB-CPU is general enough to solve complex problems. There are three machine-code instruction formats (R, I, and J type) and a total of 14 instructions.

2 COMPONENTS

- **Multiplexers:** A multiplexer (or MUX) selects between several input signals and forwards the selected input to a single output line.
- **Sign Extenders:** Sign Extender performs an operation in which the number of bits representing a specific value is increased to 16 bits by padding while preserving the original sign and value.
- **ALU:** It stands for arithmetic logic unit and performs arithmetic and logic operations. It performs the functions **ADD, SUB, MUL, AND, OR, IMP** along with **Zero (Z)** flag.
- **Left Shifter:** A Left Shifter multiplies by powers of 2. Thus, it shifts a binary number left by a specified number of positions.
- **Register File:** The RF contains 8 general purpose registers (R₀ to R₇). Register R₇ stores the Program Counter (Instruction Pointer).
- **FSM (Finite-State Machine):** Used as a mathematical model of computation, it is an abstract machine that can be in exactly one of a finite number of states at any given time. Our design has 14 states.
- **Datapath:** A datapath is a collection of functional units such as arithmetic logic units or multipliers that perform data processing operations, registers. Along with the control unit, it composes the central processing unit (CPU).

3 INSTRUCTION SET ARCHITECTURE

3.1 Instruction Formats

Opcode	R _A	R _B	R _C	Unused	Condition (CZ)
4 bits	3 bits	3 bits	3 bits	1 bit	2 bit

Table 1: R Type Instruction format

Opcode	R _A	R _C	Immediate
4 bits	3 bits	3 bits	6 bits signed

Table 2: I Type Instruction format

Opcode	R _A	Immediate
4 bits	3 bits	9 bits signed

Table 3: J Type Instruction format

3.2 Instructions Encoding

ADD	00_00	R _A	R _B	R _C	o	00
SUB	00_10	R _A	R _B	R _C	o	00
MUL	00_11	R _A	R _B	R _C	o	00
ADI	00_01	R _A	R _B	6 bit Immediate		
AND	01_00	R _A	R _B	R _C	o	00
ORA	01_01	R _A	R _B	R _C	o	00
IMP	01_10	R _A	R _B	R _C	o	00
LHI	10_00	R _A	o + 8 bit Immediate			
LLI	10_01	R _A	o + 8 bit Immediate			
LW	10_10	R _A	R _B	6 bit Immediate		
SW	10_11	R _A	R _B	6 bit Immediate		
BEQ	11_00	R _A	R _B	6 bit Immediate		
JAL	11_01	R _A	9 bit Immediate			
JLR	11_10	R _A	R _B	000_000		

4 STATE DESCRIPTIONS

4.1 S0

State Operation	Control
$PC \rightarrow Mem_Addr$	MDR
$Mem_Data \rightarrow T_1$	$T_1:E$
$PC \rightarrow ALU_A$	ADD
$+2 \rightarrow ALU_B$	
$ALU_C \rightarrow RF_D_3$	WR_EN
$X_{07} \rightarrow RF_A_3$	

4.2 S1

State Operation	Control
$r_A \rightarrow RF_A_1$	
$r_B \rightarrow RF_A_2$	
$RF_D_1 \rightarrow T_2$	$T_2:E$
$RF_D_2 \rightarrow T_3$	$T_3:E$

4.3 S2

State Operation	Control
$T_2 \rightarrow ALU_A$	
$T_3 \rightarrow ALU_B$	
$ALU_C \rightarrow T_4$	$T_4:E$
$r_C \rightarrow T_or$	$T_or:E$

4.4 S3

State Operation	Control
$T_4 \rightarrow RF_D_3$	WR_EN
$T_or \rightarrow RF_A_3$	

4.5 S4

State Operation	Control
$Imm_6 \rightarrow SE_6$	
$T_2 \rightarrow ALU_A$	ADI
$SE_6 \rightarrow ALU_B$	
$ALU_C \rightarrow T_4$	$T_4:E$
$r_B \rightarrow T_or$	$T_or:E$

4.6 S5

State Operation	Control
Imm6 \rightarrow SE6	
SE6 \rightarrow ALU_A	
T ₃ \rightarrow ALU_B	
ALU_C \rightarrow T ₄	T ₄ :E

4.7 S6

State Operation	Control
T ₄ \rightarrow Mem_Addr	MDR
Mem_Data \rightarrow T ₄	T ₄ :E
r _A \rightarrow T_or	T_or:E

4.8 S7

State Operation	Control
T ₄ \rightarrow Mem_Addr	MWR
T ₂ \rightarrow Mem_Data	

4.9 S8

State Operation	Control
T ₂ \rightarrow ALU_A	ADD
T ₃ \rightarrow ALU_B	
ALU_C \rightarrow T ₄	
ALU_F_Z \rightarrow Z_IN	
r _C \rightarrow T_or	T_or:E

4.10 S9

State Operation	Control
PC \rightarrow ALU_A	
Imm6 \rightarrow LS \rightarrow SE6	
SE6 \rightarrow ALU_B	
ALU_C \rightarrow RF_D ₃	WR_EN
X ₀₇ \rightarrow RF_A ₃	

4.11 S10

State Operation	Control
$r_A \rightarrow RF_A3$	
$PC \rightarrow RF_D3$	WR_EN

4.12 S11

State Operation	Control
$r_B \rightarrow RF_A2$	
$RF_D2 \rightarrow RF_D3$	WR_EN
$X_{07} \rightarrow RF_A3$	

4.13 S12

State Operation	Control
$Imm9 \rightarrow SE9 \rightarrow LS$	
$LS \rightarrow T_4$	$T_4:E$
$r_A \rightarrow T_or$	$T_or:E$

4.14 S13

State Operation	Control
$Imm9 \rightarrow SE9$	
$SE9 \rightarrow T_4$	$T_4:E$
$r_A \rightarrow T_or$	$T_or:E$

5 INSTRUCTION STATE-FLOW DIAGRAM


5.1 ADD/SUB/MUL/AND/OR/IMP




5.2 ADI




5.3 LHI

 


5.4 LLI

 


5.5 LW

 


5.6 SW

 


5.7 BEQ

 


5.8 JAL

 

5.9 JLR

 

6 FINITE STATE MACHINE

 

Any state in the FSM with no outward arrows has been implicitly assumed to go to S_0 upon RESET.

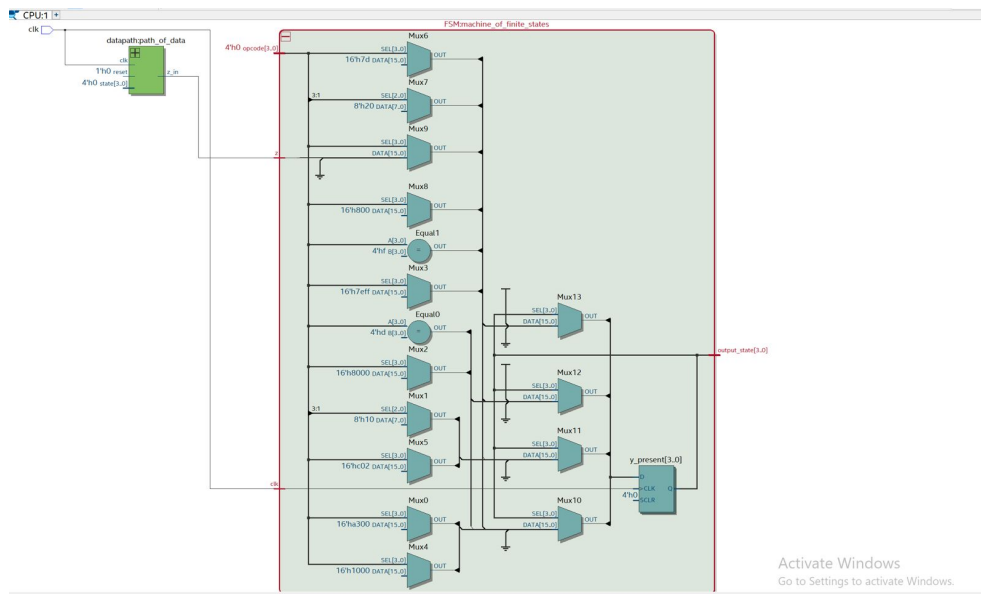


Figure 1: FSM_RTL

7 DATAPATH

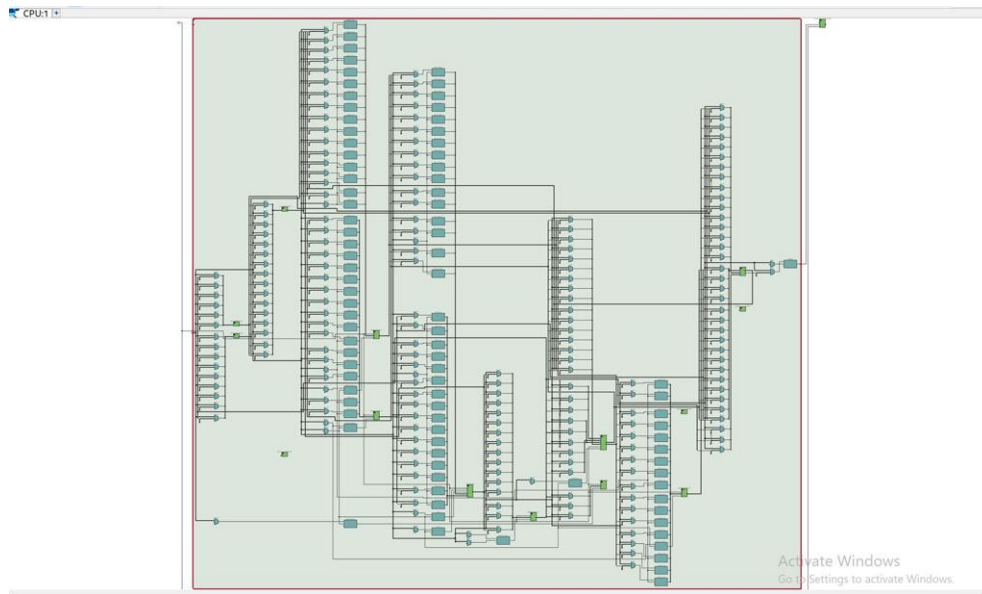


Figure 2: Data Path_NetList

8 RTL SIMULATION

 


Figure 3: CPU_Testing

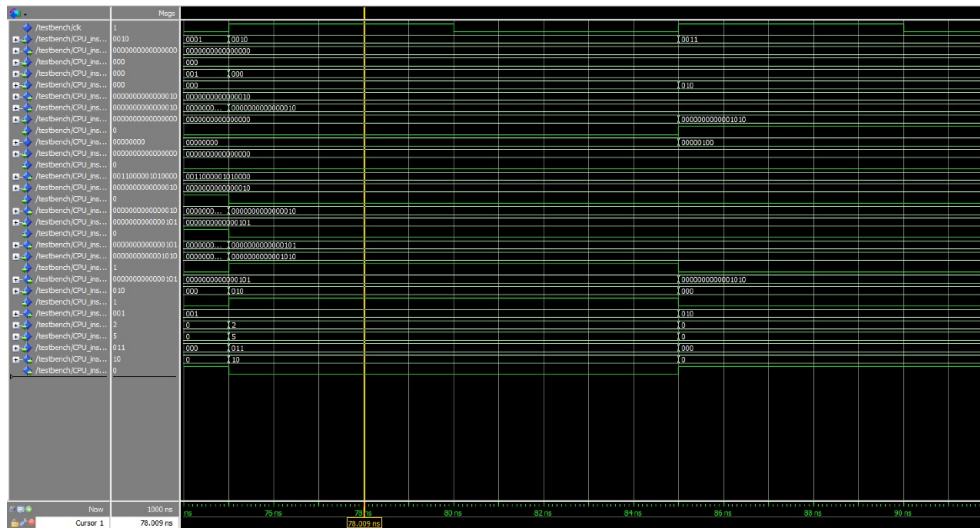


Figure 4: CPU_Testing

9 CONCLUSION

- Thus using an FSM of 14 states, we implemented 14 instructions each of which can be distinguished using the given op-codes and the Z bit.
- The implementation of the DataPath was achieved by utilizing the state and clock as inputs. This resulted in outputs that included the interconnections among various components and the status of control signals (such as memory read enable, memory write enable, Program Register write enable, etc.) relevant to that state.
- The entity CPU was designed including both the FSM and the DataPath using the clock as input.

10 MEMBER CONTRIBUTIONS

- **Aaditya Gupta (22B3941)**: Responsible for creating some of the Components and also helped in designing FSMs for the report.
- **Dattaraj Salunkhe (22B1296)**: Implemented the logic and testing of Datapath and helped in integration of the CPU.
- **Harsh Sanjay Roniyar (22B3942)**: Created the State Transition tables and integrated the individual state-flow diagrams into the FSM. Also, created the report and in the integration of the CPU.
- **Pranav Prakash (22B3945)**: Implemented the crucial memory blocks and also integrated the Components together in the CPU. Also, helped in designing the State Transition tables.